

Alexander & Sadiku Example Problem 10.6
Michael Gustafson

> restart

Handy functions for dealing with phasors

> $j := I$:

> $polard := (mag, angd) \rightarrow polar(mag, angd * Pi / 180)$:

> $argumentd := (num) \rightarrow argument(num) * 180 / Pi$:

> $listphasors := \text{proc}(plist) \text{ local } k$
for k **from** 1 **to** $nops(plist[])$ **do**
 $printf("%s = \%f < \%f \text{ deg}\backslash n", lhs(plist[][k]), evalc(abs(rhs(plist[][k]))),$
 $evalc(argumentd(rhs(plist[][k])))$)
end do end proc:

Circuit equations

> $KCLn2 := \frac{(Vn2 - Va)}{j\omega \cdot L} - Ib + \frac{Vo}{R1} = 0$:

> $KCLn3 := -\frac{Vo}{R1} + j\omega \cdot C \cdot (Vn2 - Vo) + \frac{(Vn2 - Vo - Vc)}{R2} = 0$:

Solve circuit equations

> $MySoln := solve(\{KCLn2, KCLn3\}, [Vn2, Vo])$:

> $collect(MySoln, j\omega)$

$$\left[\left[\begin{aligned} Vn2 = & (C Ib L R1 R2 j\omega^2 + (C R1 R2 Va + Ib L R1 + Ib L R2 + L Vc) j\omega \\ & + R1 Va + R2 Va) / (C L R2 j\omega^2 + (C R1 R2 + L) j\omega + R1 + R2), Vo \\ = & \frac{R1 (C Ib L R2 j\omega^2 + (C R2 Va + Ib L) j\omega + Va - Vc)}{C L R2 j\omega^2 + (C R1 R2 + L) j\omega + R1 + R2} \end{aligned} \right] \right] \quad (1)$$

Define lists for elements, then for each frequency independently

> $ElVals := R1 = 1, R2 = 4, L = 2, C = 0.1$:

> $Valsa := ElVals, j\omega = j \cdot 2, Va = polard(10, 0), Ib = 0, Vc = 0$:

> $Valsb := ElVals, j\omega = j \cdot 5, Va = 0, Ib = polard(2, -90), Vc = 0$:

> $Valsc := ElVals, j\omega = j \cdot 0, Va = 0, Ib = 0, Vc = polard(5, 0)$:

Find solutions for each frequency

> $MySolna := subs(Valsa, MySoln)$:

> $MySolnb := subs(Valsb, MySoln)$:

> $MySolnc := subs(Valsc, MySoln)$:

Find phasors for each frequency

> $listphasors(MySolna)$

$Vn2 = 9.877484 < -60.353678 \text{ deg}$

$Vo = 2.498097 < -30.784147 \text{ deg}$

> $listphasors(MySolnb)$

$Vn2 = 5.606810 < -119.538782 \text{ deg}$

$Vo = 2.328101 < -77.905243 \text{ deg}$

> $listphasors(MySolnc)$

$V_{n2} = 0.000000 < 0.000000 \text{ deg}$
 $V_o = 1.000000 < 180.000000 \text{ deg}$

>

Conclusion:

$$v_o(t) = 2.498 \cos(2 t - 30.78 \text{ deg}) + 2.328 \cos(5 t - 77.91 \text{ deg}) - 1$$